

Soft-Error Analysis

Patrick Klampfl


February 1st, 2017

Overview

- Introduction:
 - Soft-Errors
 - Protection Logic
 - Classification of components
- Techniques:
 - simulation vs. formal vs. semi-formal
- Algorithms (application of the techniques for classification)
- Benchmark Results

Soft Errors / Faults

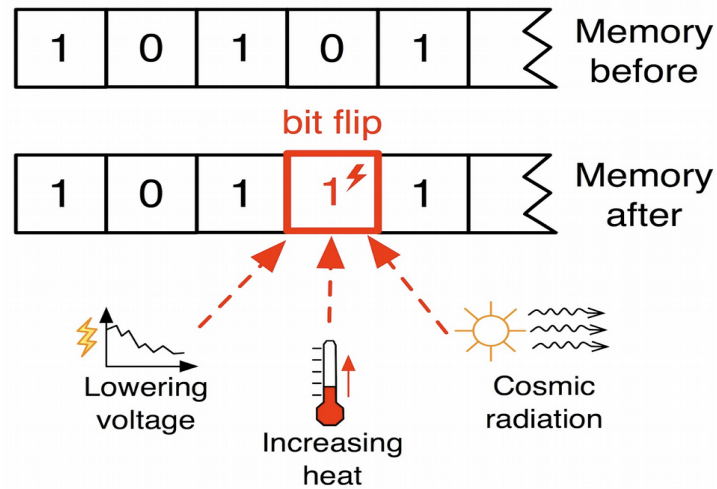- Sequential Boolean Circuits: inputs, AND gates, latches, outputs
- Components (latches, AND gates) can suffer from faults
 - flip truth value
- Single fault assumption




Protection Logic

- Special part of a circuit for reliability
- Detect faults or correct faults
- Examples: Triple Modular Redundancy (TMR), parity-checks, ...


How to **correct** errors: TMR Example

- Example: triple modular redundancy

 


- Con: > 200% overhead in power consumption and area!

How to **detect** errors?

 


How to detect errors:

- → add **redundancy**.

 


Errors in protection logic

 - vulnerable latches
 - Faults that corrupt primary outputs
→ soft error escaped




 - false positives
 - Unnecessarily reported faults




Techniques for Component Classification

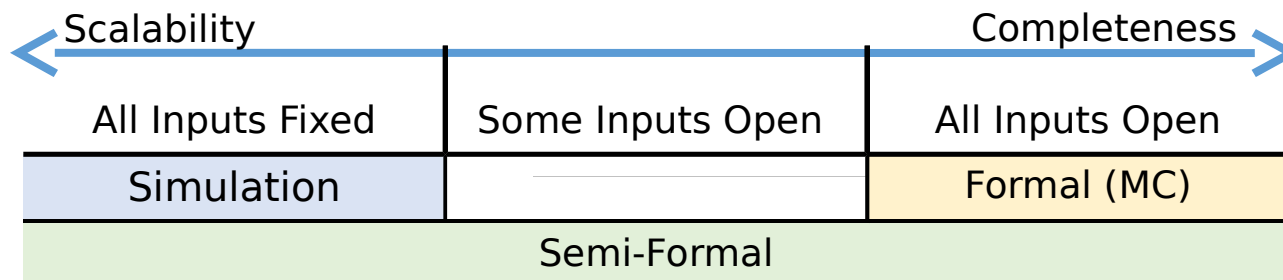- Formal methods
 - Complete
 - Slow, bad scalability
- Simulation
 - Not Complete
 - Fast, good scalability
- Semi-Formal methods
 - Flexible




Detecting **vulnerable** latches

 

- Formal method: (Bounded) Model Checking
- Simulation
- Semi-formal methods

Formal: Model Checking Approach

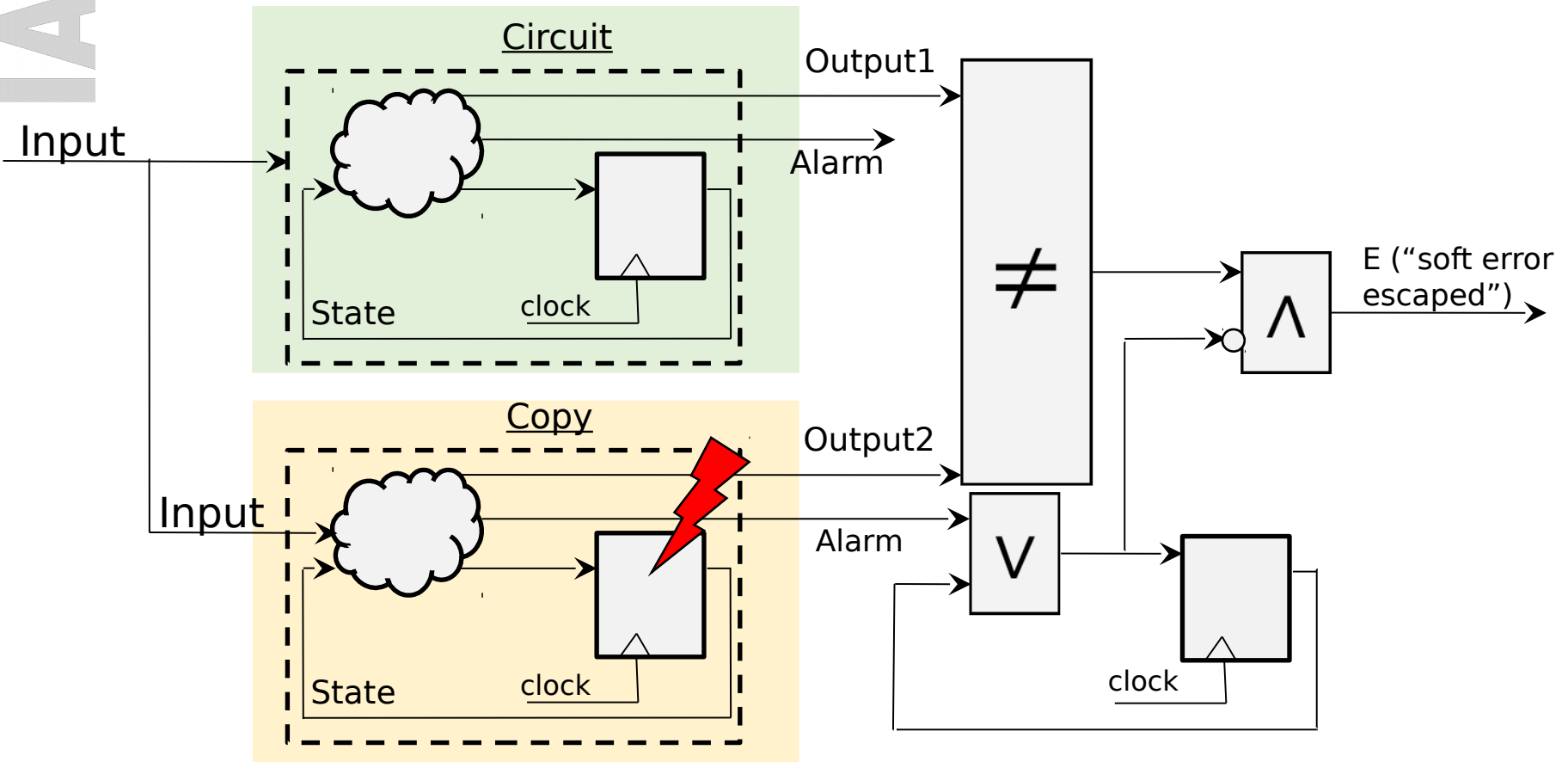

Simulation (1/2)

- Test case provides input values for the circuit:

```
01101000110  
10101100111  
...
```

(1) Execute **correct** simulation

(2) Execute **faulty** simulations

- Induce faults
- Compare output values with correct simulation

```
for all latches l in L:  
  for all time steps i=1 to len(t):  
    // check if soft error injected at  
    // latch l in step i of test case t  
    // escapes (now or in future steps)
```

Simulation (2/2)

- **Not complete!** (only concrete test cases)
- But: might already find some **vulnerable** latches / **false positives**
- Fast for a **single** test case
- Not suited for **verification**

Semi-Formal approach

- Sequential Equivalence Checking
- SAT-based: symbolically encode the circuit as a formula
- test case-based: Input values from test cases, can be concrete or open


```
011??01000110  
101??01100111  
...
```

- point in time AND component to flip symbolic


```
for all latches l in L:  
  for all time steps i=1 to len(t):  
    Flip latch  
    //check ...
```

Convert circuit to CNF formula (for SAT-solver)

 - Circuit can be converted to a transition relation formula $T(\bar{x}, \bar{i}, \bar{o}, \bar{x}')$
 - talks about **inputs**, **outputs**, **current-** and **next state**
- Execution of circuit: $T(\bar{x}_0, \bar{i}_0, \bar{o}_0, \bar{x}_1) \wedge T(\bar{x}_1, \bar{i}_1, \bar{o}_1, \bar{x}_2) \wedge \dots \wedge T(\bar{x}_n, \bar{i}_n, \bar{o}_n, \bar{x}_{n+1})$



0: 01 0
 1: 1? ?
 ...
 n: ?? ?

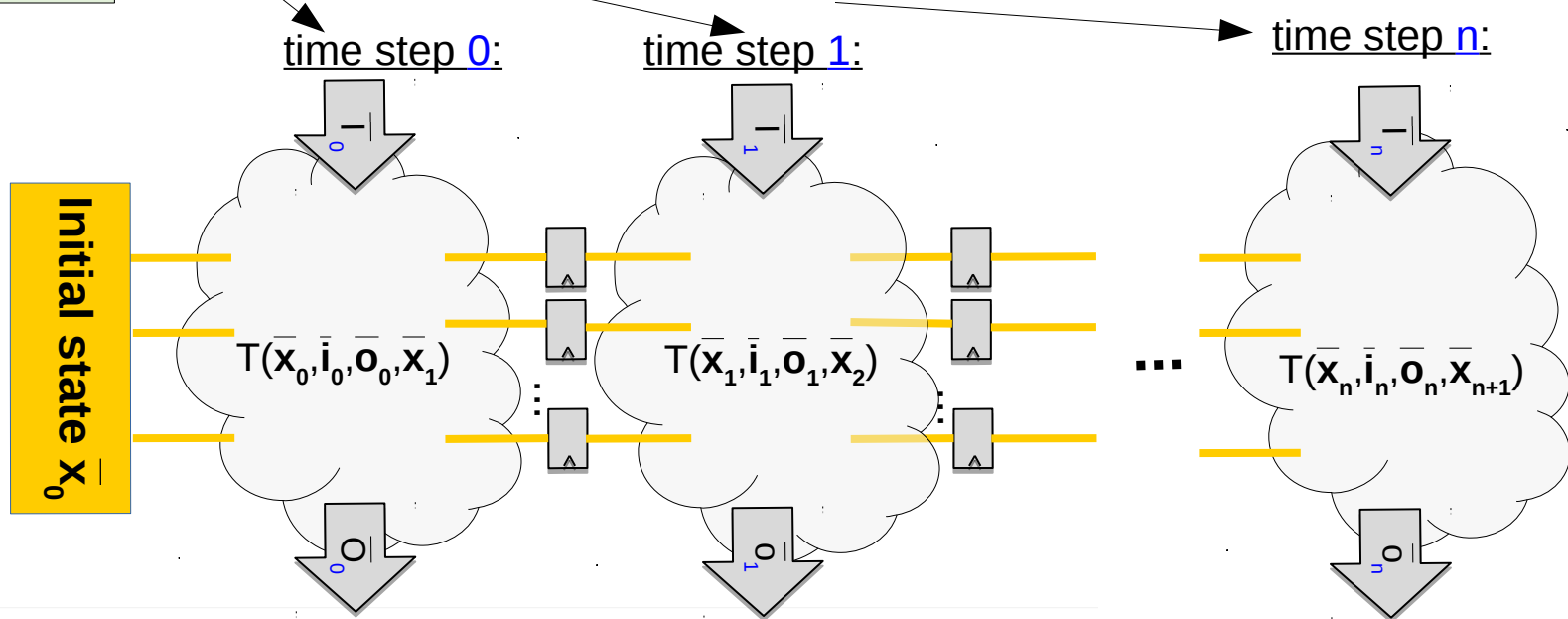

Semi-Formal Algorithm

- Sequential Equivalence Checking: compare **fault-free** and **faulty** circuit
- SAT-based: symbolically encode the execution of both circuits as a formula:
 - **fault-free**: $T(\bar{x}_0, \bar{i}_0, \bar{o}_0, \bar{x}_1) \wedge T(\bar{x}_1, \bar{i}_1, \bar{o}_1, \bar{x}_2) \wedge \dots \wedge T(\bar{x}_n, \bar{i}_n, \bar{o}_n, \bar{x}_{n+1})$
 - **faulty**: $T(f_0, \bar{c}, \bar{x}'_0, \bar{i}'_0, \bar{o}'_0, \bar{x}'_1) \wedge T(f_1, \bar{c}, \bar{x}'_1, \bar{i}'_1, \bar{o}'_1, \bar{x}'_2) \wedge \dots \wedge T(f_n, \bar{c}, \bar{x}'_n, \bar{i}'_n, \bar{o}'_n, \bar{x}'_{n+1})$
 - \bar{c} defines **which** latch should be flipped, \bar{f} defines the point in time **when** it should be flipped
- test case-based: Input values \bar{i} from test cases, can be concrete or open

```
011??01000110
101??01100111
...
```


SAT-query to find vulnerable components


```
for all time steps i=1 to len(t):  
    "Dear SAT solver, can you produce a wrong output at step i without  
    alarm raised by flipping any latch in some earlier step?"
```

- If SATISFIABLE:

assignment: $\neg f_0$, **f**₁, $\neg f_2$, .. , $\neg f_n$, $\neg c_1$, $\neg c_2$, **c**₃, .. , $\neg c_m$


- **c**₃: Latch **3** is flipped
 ...
- **f**₁: it is flipped in time step **1**
- Output wrong in step **i** (at query time)

Detecting definitely protected latches

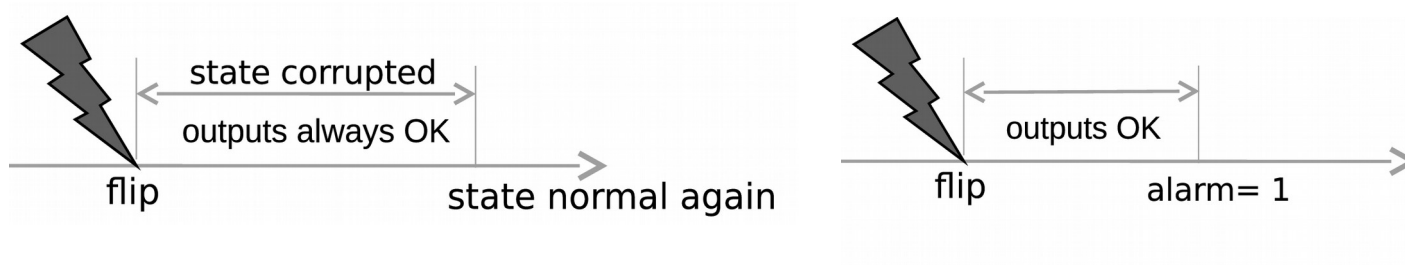

- must hold in **any** state!
- Definitely protected → not vulnerable
- Not definitely protected → ??? (maybe protected, maybe vulnerable..)


Detecting definitely protected latches

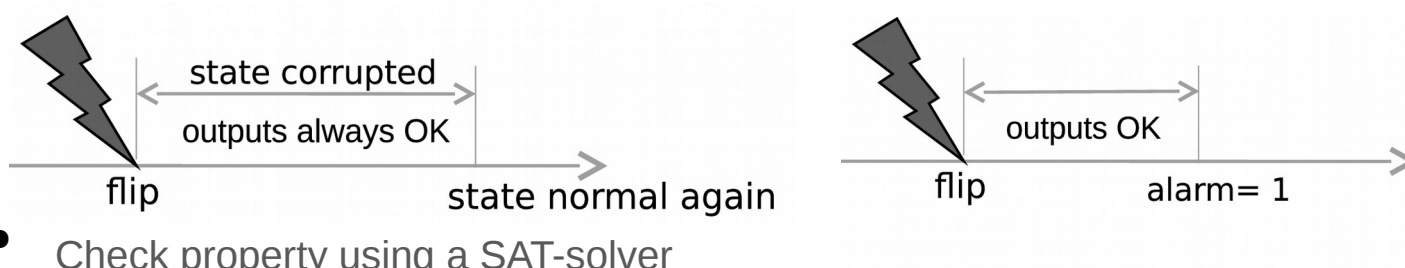


- Check property using a SAT-solver
- **k-step protection** of a latch:
A fault in **any** state (an over-approximation of all states) ...
 - a) ... either gets masked out within at most **k** time steps
(and does not affect any outputs)
 - b) ... or an alarm is raised within at most **k** time steps
(and does not affect any outputs before)

False Positives

 
- Problem: impossible to compare outputs **forever**
 - undecidable



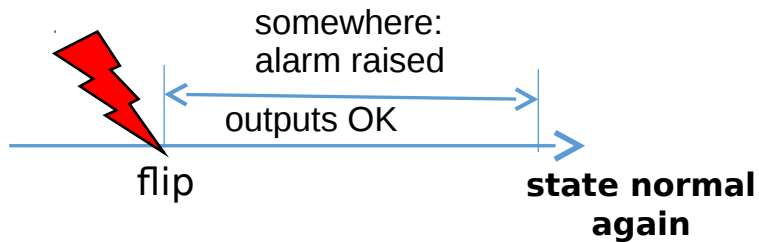- Solution: search for situations where the state is repaired within finite time
 - Incomplete: might not find all false positives



Detecting false-positives

 

- Formal method: (Bounded) Model Checking
- Simulation
- Semi-formal methods

SAT query to find false positives

- Find situations where
 - bit flip raises an alarm, does not corrupt outputs, and state recovers from bitflip

```
for all time steps i=1 to len(test-case):  
    "Dear SAT solver, can you find a false positive by flipping  
    any latch in any previous time step?"
```


- If SATISFIABLE: false positive found

assignment: $\neg f_0$, **f**₁, $\neg f_2$, .. , $\neg f_n$, $\neg c_1$, $\neg c_2$, **c**₃, .. , $\neg c_m$

- **c**₃: Latch **3** has to be flipped
- **f**₁: it has to be flipped in time step **1**
- state ok again in step **i** (at query time)

Summary

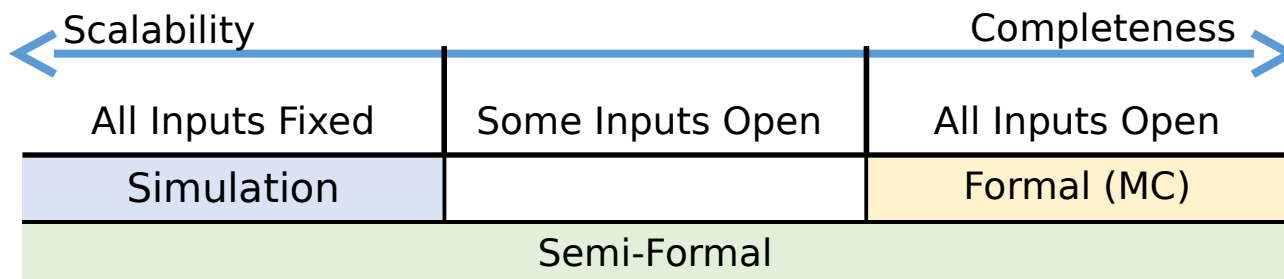
- Properties to check
 - Search for **vulnerable** components
 - Prove that component is **definitely protected**
 - Find situations for **false positives**
- Techniques for checking:



Results – simulation vs semi-formal (1/2)

- Simulation vs semi-formal (**point in time** and **component** to flip are symbolic variables)
- 3 **concrete** test cases, each 15 time steps long
- Search for **vulnerable** latches


 
```
011010001110  
101011010111  
...
```



Results – simulation vs semi-formal (2/2)

- 3 test cases, each 15 time steps long, containing some **open** input values
- Search for **vulnerable** latches
- >5 open inputs: **semi-formal faster**, < 5: simulation faster, ~5: about the same
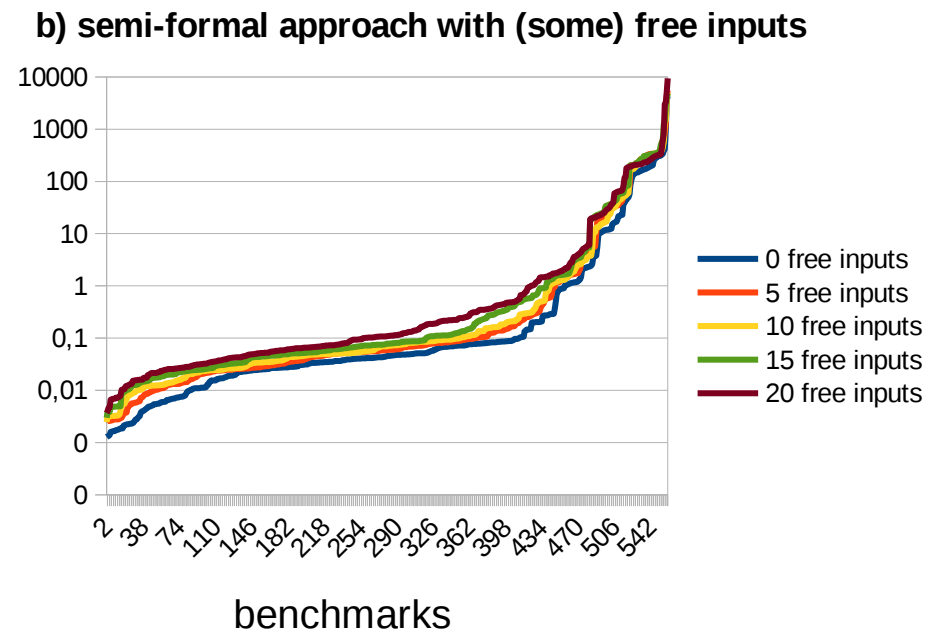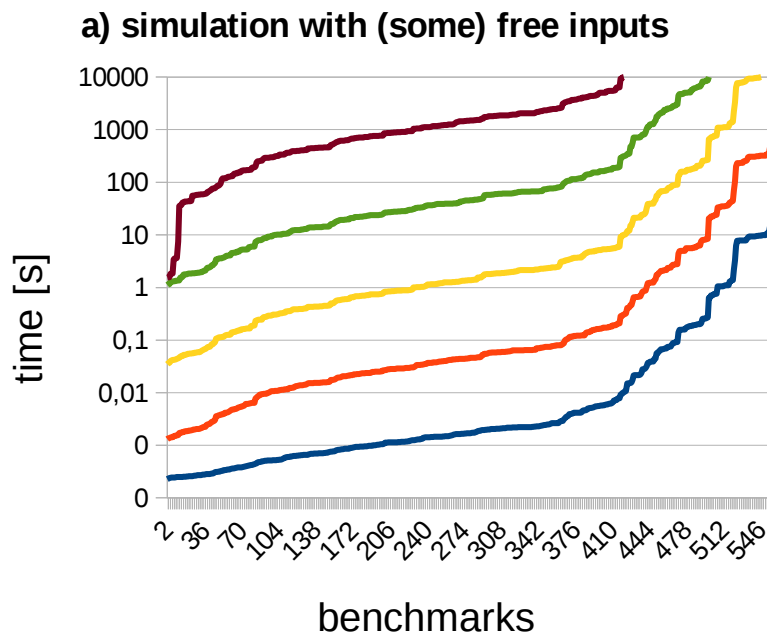
```
011??01000110  
10101??110111  
...
```





Conclusion

- Open inputs: Semi-formal algorithms scale significantly better than simulation
- Concrete Inputs: Simulation is fastest
- Reducing input space: better than MC

```
011??01000110  
10101??110111  
...
```




Thank you for your attention!
Questions?

-
- Figure 1 is a line graph showing the performance of the BLIMC MC algorithm across various benchmarks. The Y-axis represents time in seconds on a logarithmic scale from 0 to 10,000. The X-axis represents benchmarks from 2 to 542. Three data series are plotted: 'semi-formal (concrete)' (blue line), 'formal (BLIMC MC)' (red line), and 'semi-formal (all inputs open)' (yellow line). The 'semi-formal (concrete)' series shows the lowest execution times, while the 'semi-formal (all inputs open)' series shows the highest. The 'formal (BLIMC MC)' series falls in between. Annotations include a green box with red question marks and an ellipsis for benchmarks 262-422, and another green box with binary strings and an ellipsis for benchmarks 422-542.

OpenSEA

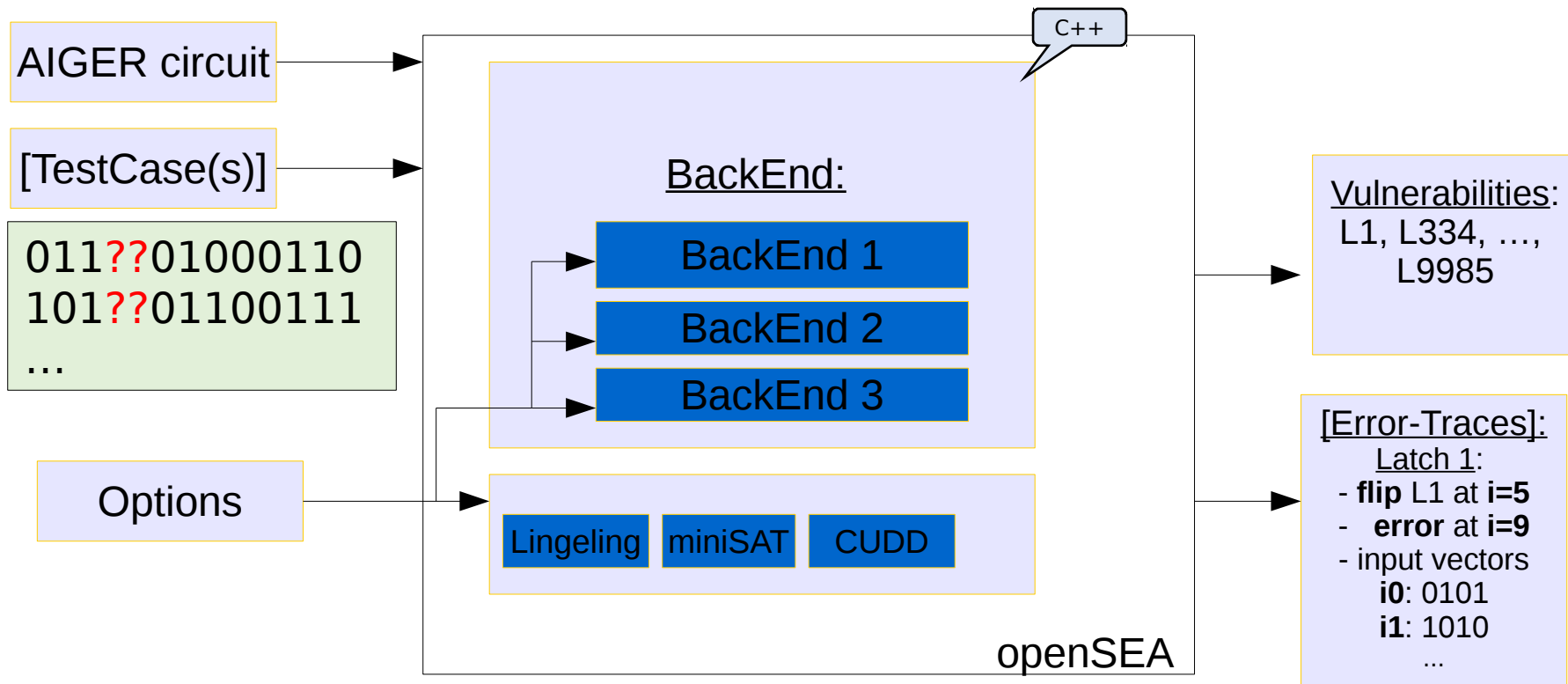- Input: arbitrary circuit with protection logic (alarm output)
- Output: List of definitely vulnerable latches



Simulation (3/3)

Simulation-based solution: Details

```
// Step 1: fault-free simulation
for all test cases t in T:
  s := initial state
  for all time steps i=1 to len(t):
    correctState[t][i] := s
    s,o := sim1step(s,t[i])
    correctOutput[t][i] := o
```

```
// Step 2: simulation with faults:
for all latches l in L:
  for all test cases t in T:
    for all time steps i=1 to len(t):
      s := correctState[i]
      s := s with L flipped
      for all time steps j=i to len(t):
        if(s == correctState[t][j])
          continue with next step i
        s,o,c := sim1step(s,t[i])
        if(alarm)
          continue with next step i
        if(o != correctOutput[t][j])
          print "Latch L is vulnerable"
          continue with next latch l
```

Semi-Formal approach

- SAT-based: symbolically encode the circuit as a formula
- test case-based: Input values from test cases, can be concrete or open

```
011??01000110
101??01100111
...
```

- 2 variants:

- A) point in time to flip symbolic:

```
for all test cases t in T:
  for all latches l in L:
    for all time steps i=1 to len(t):
      // check ...
```


- B) point in time AND component to flip symbolic

```
for all test cases t in T:
  for all latches l in L:
    for all time steps i=1 to len(t):
      // check ...
```


A) point in time to flip symbolic:

```
for all test cases t in T:  
  for all latches l in L:  
    for all time steps i=1 to len(t):  
      // check ...
```

timestep 0:

 



timestep 1:

 

- If SATISFIABLE: assignment: $\neg f0$, **$f1$** , $\neg f2$, .. , $\neg fn$
 - Flip L in step 1 to produce corrupt outputs

Environment Models

  
- Output values might be irrelevant
 - e.g. if data on bus is not ready
- Some input combinations might not be allowed
 - SAT-solver choices for input values can be restricted



Results – Length of Test Cases


STLA - 90% protected

execution with different input-lengths

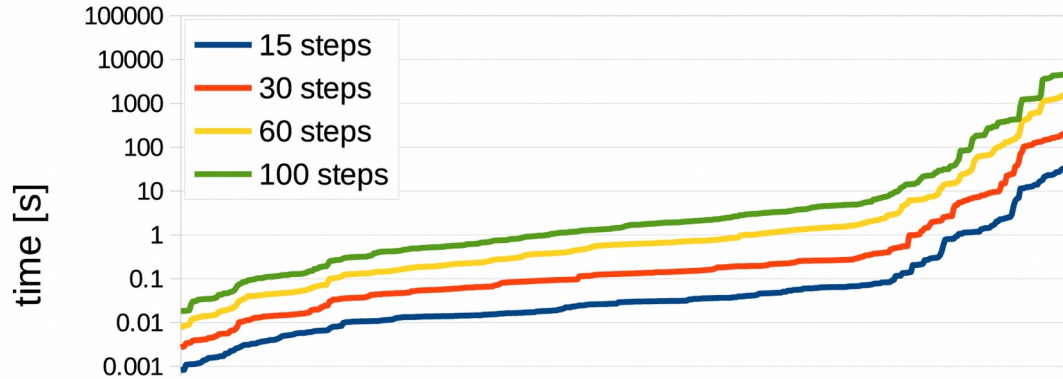


SIM - 90% protected

execution with different input-lengths

 

Vulnerable Latches:


- Given: circuit

 

→ time


Vulnerable Latches:

- Given: circuit

 


- Find situation..

- where Latch can be flipped ...

 

Vulnerable Latches:

- Given: circuit

 

- Find situation..

- where Latch can be flipped ...
- such that outputs are wrong
- without raising an alarm before

